

SSN College of Engineering
Dept of Computer Science and Engineering
UCS1301: Digital Principles System Design


1. A Sequential circuit has **two JK flip flops A and B**, **two inputs x and y**, and **one output Z**. The flip flops input equations and circuit output equation are

$$\begin{aligned} \mathbf{JA} &= \mathbf{Bx + B'y'} & \mathbf{KA} &= \mathbf{B'xy'} \\ \mathbf{JB} &= \mathbf{A'x} & \mathbf{KB} &= \mathbf{A + xy'} \\ \mathbf{Z} &= \mathbf{Ax'y' + Bx'y'} \end{aligned}$$

- i. Draw the logic diagram of the circuit.
- ii. Derive the state equations for A and B.
- iii. Tabulate the state table.
- iv. Draw state diagram

2. Design a sequential circuit with two *JK* flip-flops A and B and two inputs E and F . If E = 0, the circuit remains in the same state regardless of the value of F . When E = 1 and F = 1, the circuit goes through the state transitions from 00 to 01, to 10, to 11, back to 00, and repeats. When E = 1 and F = 0, the circuit goes through the state transitions from 00 to 11, to 10, to 01, back to 00, and repeats.

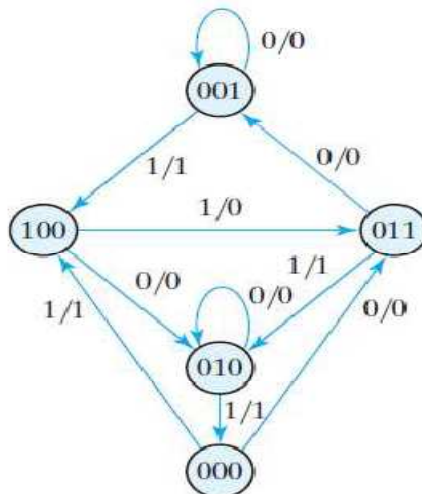3. A sequential circuit has three flip-flops A, B, C ; one input *x_{in}* ; and one output *y_{out}* . The state diagram is shown in the below figure. The circuit is to be designed by treating the unused states as don't-care conditions. Analyse the circuit obtained from the design to determine the effect of the unused states. Design using T flip Flop.



4. Design a BCD to 2421 code convertor using PROM , PAL, and PLA.